

* RDS is the most important concept in the whole of science and engineering (and in life?) ...

* Remember Physics 101: Circuits in parallel or in series!

$$i = \frac{V}{R_{eq}} ; \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$i = \frac{V}{R_{eq}} ; R_{eq} = R_1 + R_2$$

vs.

∴ Conductances are additive!


∴ Resistances are additive!

$$\underline{i = (C_1 + C_2) V}$$

$$\underline{i = \frac{V}{R_1 + R_2}}$$

...analogous to...


* Two parallel rxns:

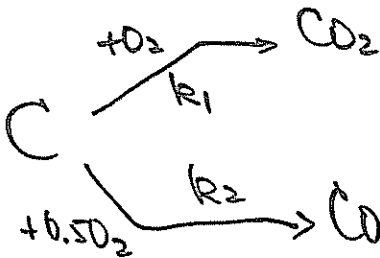

$$\text{Rate} = (R_1 + R_2) C_{\text{O}_2}$$

[Assuming both rxns zero order w/r to C and 1st order w/r to O₂]

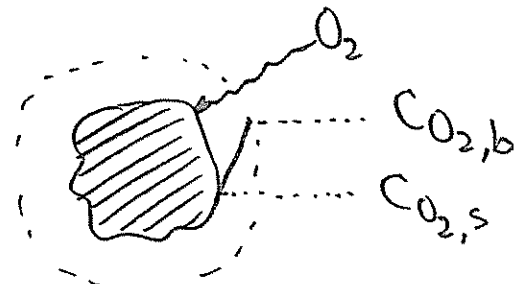* Diffusion to the surface followed by rxn on the surface:



$$\text{Rate of diffusion} = R_d (C_{\text{O}_2,b} - C_{\text{O}_2,s})$$

$$\text{Rate of surface rxn} = R_r C_{\text{O}_2,s}$$

$$\therefore \text{Rate} = \frac{C_{\text{O}_2,b}}{\frac{1}{R_r} + \frac{1}{R_d}} \quad (\text{Show!})$$

...EXTRA CREDIT...